

74LS245 octal bidirectional bus buffers;
and the control bus signals, M>IO, RD,
and WR use a 74LS244 buffer.
A fully buffered 8086 system requires
one 74LS244, two 74LS245s,
and three 74LS373s.
The 8086 requires one more buffer
than the 8088 because of the extra
eight data bus connections, D15-D8.
It also has a BHE signal that is buffered
for memory-bank selection.

depicts a fully buffered 8088 microprocessor. Notice that the remaining eight address pins, A15–A8, use a 74LS244 octal buffer; the eight data bus pins, D7–D0, use a 74LS245 octal bidirectional bus buffer; and the control bus signals, M>IO, RD, and WR, are buffered.

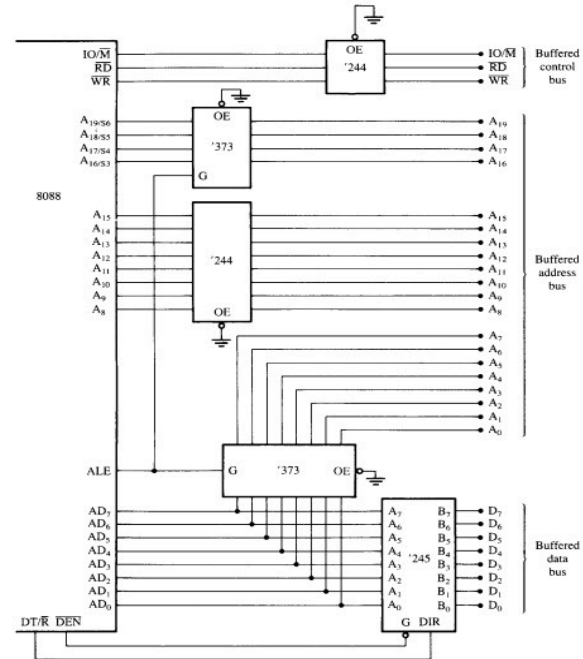


FIGURE 9-7 A fully buffered 8088 microprocessor.